


模电作业.2

2025年9月5日

22:53

自动化2406 迟泰炎U202414215

2.3.4

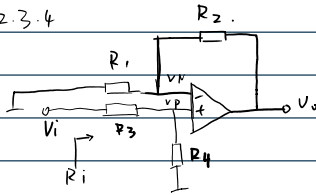

$$(1) \begin{cases} \frac{V_i - V_P}{R_3} = \frac{V_P}{R_4} \\ \frac{V_P - V_P}{R_2} = \frac{V_P}{R_1} \end{cases}$$

$$\therefore A_v = \frac{V_o}{V_i} = \frac{\frac{R_1 R_2}{R_3 + R_4}}{\frac{R_1 R_2}{R_3 + R_4}} = \frac{R_4 (R_1 + R_2)}{R_1 (R_3 + R_4)}$$


$$R_i = \frac{V_i}{I_i} = \frac{\frac{R_1 R_2}{R_3 + R_4} V_P}{\frac{V_P}{R_4}} = R_3 + R_4$$

$$(2). \pm 10 \pm 2$$

$$\therefore \pm 12 \text{ V 左右}$$

$$(3). R = \frac{4}{I} = \frac{10}{(20 - 0.5) \times 10^{-3}} \approx 513 \Omega$$

2.3.7

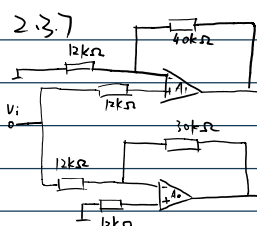

$$(1). V_i = 0.5 \sin \omega t$$


$$V_{01} = (1 + \frac{40k}{12k}) V_i \approx 2.17 \sin \omega t$$

$$V_{02} = (-\frac{30k}{12k}) V_i = -1.25 \sin \omega t$$

$$V_o = V_{01} - V_{02} = 3.42 \sin \omega t$$

$$(2). A_v = \frac{V_o}{V_i} = \frac{3.42 \sin \omega t}{0.5 \sin \omega t} = 6.84$$

$$R_i = 12 \Omega$$

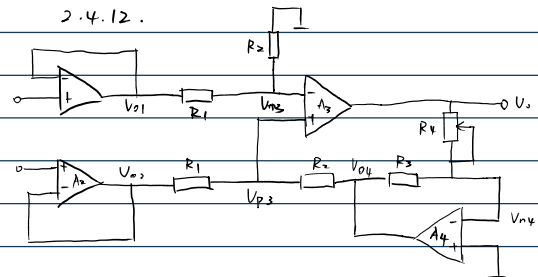

$$\text{增益 } A_v = \frac{V_o}{V_{i1} - V_{i2}}$$

$$V_{01} = V_{i1}, V_{02} = V_{i2}, V_{03} = V_{01}$$

$$V_{04} = -\frac{R_3}{R_4} V_{03}$$


$$\frac{V_{01} - V_{03}}{R_1} = \frac{V_{01}}{R_2}$$

$$\frac{V_{02} - V_{03}}{R_1} = \frac{V_{02} - V_{04}}{R_2}$$

$$R_2 V_{01} - R_2 V_{02} = V_{03} \frac{-R_1 R_2}{R_2}$$

$$\therefore A_v = \frac{V_o}{V_{i1} - V_{i2}} = -\frac{R_2 R_4}{R_1 R_3}$$

2.3.10

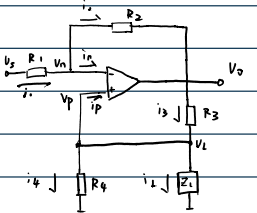

$$\frac{R_2}{R_1 R_3} = \frac{1}{R_4}$$


$$V_n = V_p = V_L = i_L \cdot Z_L$$

$$\frac{V_0 - V_n}{R_1} = \frac{V_n - V_0}{R_2}$$

$$\frac{V_0 - V_L}{R_3} = i_L + \frac{V_L}{R_4}$$

$$\therefore \frac{i_L}{V_0} = -\frac{1}{R_4}$$

2.3.11

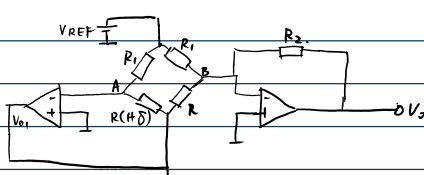

$$V_0 \sim \delta$$


$$U_A = U_B = 0$$

$$\text{对A列KCL: } \frac{V_{01} - 0}{R_1} = \frac{0 - V_{REF}}{R_1}$$


$$\text{对B列KCL: } \frac{V_0 - 0}{R_2} + \frac{V_{REF} - 0}{R_1} = \frac{0 - V_0}{R_1}$$

$$\text{联立得: } V_0 = \frac{R_2}{R_1} \cdot V_{REF} \cdot \delta$$

2.4.4

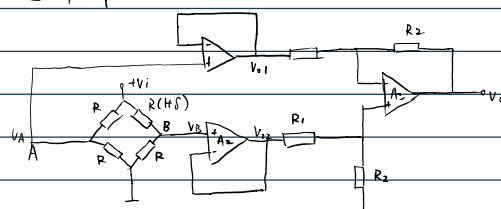

2.4.15

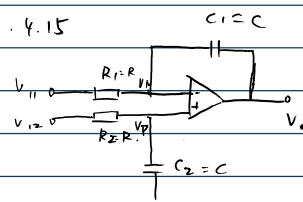

$$(1). V_p(s) = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_{i2}(s)$$

$$V_o'(s) = \left[1 + \frac{\frac{1}{sC}}{R} \right] V_p(s)$$


$$= \frac{1}{sCR} V_{i2}(s) = \frac{1}{RC} \int_0^t V_{i2} dt$$


$$(2). V_o''(s) = -\frac{1}{sRC} V_{i1}(s)$$

$$V_o' = -\frac{1}{RC} \int_0^t V_{i1} dt$$

$$(3). V_o = V_o' + V_o'' = \frac{1}{RC} \int_0^t (V_{i1} - V_{i2}) dt$$

2.4.18

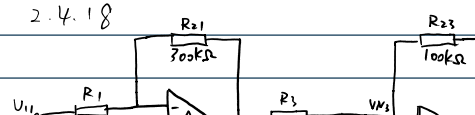

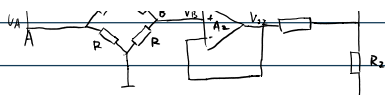

$$(1). \quad V_{o1} = V_A = \frac{V_i}{2} \quad V_{o2} = \frac{R}{2R+8R} \cdot V_i = \frac{1}{2+8} V_i$$

$$V_o = \frac{R_1}{R_1} (V_{o2} - V_{o1}) = \frac{R_2}{R_1} \left(\frac{1}{2+8} - \frac{1}{2} \right) V_i = \frac{R_2 V_i}{R_1} \frac{-8}{4+28}$$


$$(2) \quad V_A = \frac{1}{2} V_i = 3.75 V$$

$$V_B = \frac{1}{2+8} V_i = 3.73 V$$

$$V_{AB} = 0.02 V$$

$$V_i = \frac{R_2}{R_1} V_i \frac{-8}{4+28} = -0.02 \frac{R_2}{R_1}$$

(3). 降低

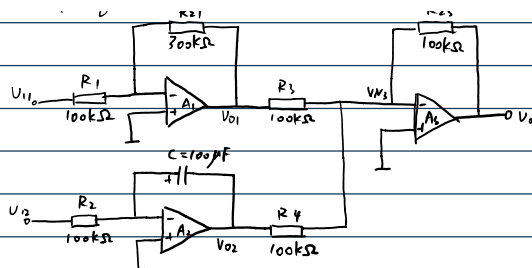

$$(1). \quad \frac{V_{11} - 0}{100k} = \frac{0 - V_{o1}}{300k}$$

$$V_{o1} = -3V_{11}$$

$$0 - V_N = \frac{1}{C} \int i_1 dt$$


$$V_{o2} = -\frac{1}{RC} \int V_{12} dt$$

$$\frac{V_{o1} - V_{N2}}{R_3} + \frac{V_{o2} - V_{N3}}{R_4} = \frac{V_{N3} - V_o}{R_{23}}$$

$$V_o = 3V_{11} + \frac{1}{RC} \int V_{12} dt$$

$$= 3V_{11} + 0.1 \int V_{12} dt$$

$$(2). \quad V_{11} = -0.1 V \quad 3V_{11} = -0.3 V$$


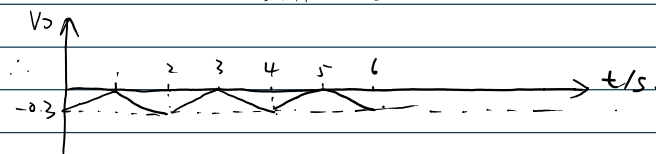


模电作业.3


2025年9月20日 16:30

U2024/14215 迟养炎 自动化2406.

3.4.3.

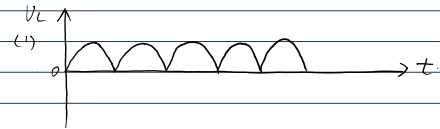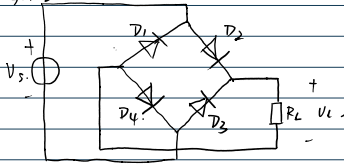

(2)

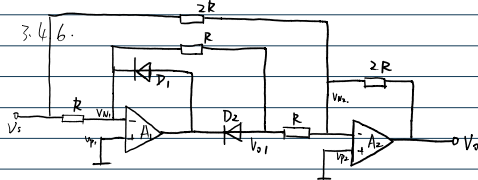


(1). 当 $V_s > 0$ 时, D_1 截止 D_2 导通.

$$V_{D1} = -V_s$$

$$V_o = -\frac{2R}{2R} V_s - \frac{1R}{R} V_a = -V_s - (-V_s) = V_s \quad (V_s > 0)$$


$$V_s \leq 0 \text{ 时, } V_{D1} = 0$$

$$V_o = -\frac{2R}{2R} V_s = -V_s$$

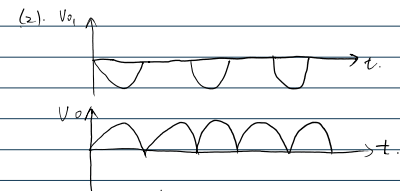

(3) 3.4.3 V_o 始终为 0

3.4.7

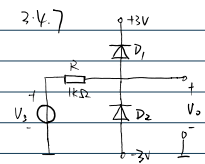


$$V_o = 6 \sin \omega t$$


$$V > 3.7: D_1 \text{ 通}$$

$$V < -3.7: D_2 \text{ 通}$$
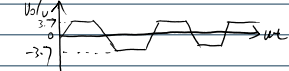
$$-3.7 \leq V \leq 3.7: D_1, D_2 \text{ 均截止, } V_o = V_s$$




3.4.13.

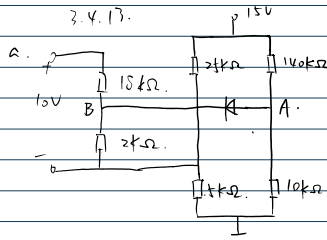

$$V_A = 1V$$

$$V_B = \frac{2}{18+2} \times 10 + \frac{5}{25+5} \times 15 = 3.5V$$


$\therefore D_1$ 截止

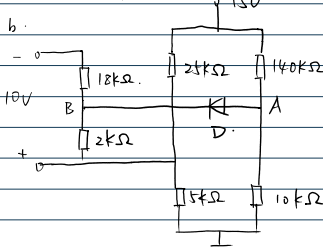



$$V_A = \frac{10k\Omega}{150k\Omega} \times 15 = 1V$$

$$V_B = -\frac{2}{18+2} \times 10 + \frac{5}{25+5} \times 15 = 1.5V$$


$\therefore D_2$ 截止

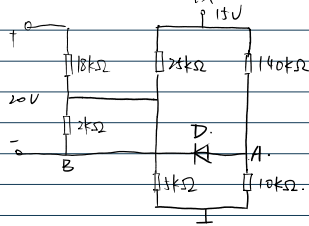

3.5.1.

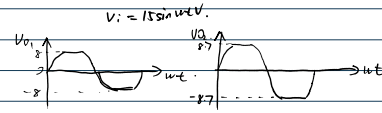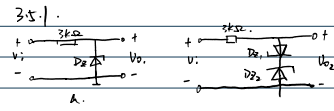

3.5.3.

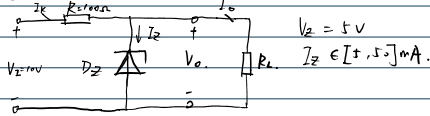

$$(1) I_R = \frac{V_E - V_Z}{R} = \frac{10-5}{100} = 0.05A$$

$$I_R - I_{om} = I_{Zmin}$$

$$0.05 - I_{om} \geq 5 \times 10^{-3}$$


$$\therefore I_{om} < 0.045A$$

$$(2) P_{DM} = I_{om} \times V_Z = 0.225W$$

$$(3) P_{ZM} = V_Z \cdot I_{Zmax} = 1 \times 5 \times 10^{-2} = 0.25W$$

$$P_{DM} = (V_i - V_Z) I_{Zmax} = (10-5) \times 5 \times 10^{-2} = 0.25W$$

3.4.14.

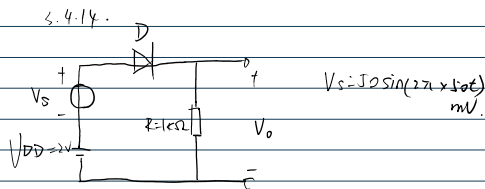

$$(1) \therefore V_D = 0.7V$$

$$\therefore I = \frac{2-0.7}{1k} = 1.3 \times 10^{-3}A$$

$$V_o = I \cdot R = 1.3V$$

(2).

$$r_d = \frac{V_T}{I_D} = \frac{26 \times 10^{-3}}{1.3 \times 10^{-3}} = 20\Omega$$

$$\therefore v_d = \frac{V_s}{R+r} = \frac{50 \times 10^{-3}}{1020} \approx 0.049V$$

$$(3) v = V_1 + V_2 = 1.3 \times 10^{-3} + 0.049 \sin(2\pi \times 50t) V$$

2025年10月8日 16:48


4.1.1 4.2.1 4.4.3 4.4.4 4.5.2 4.5.5 (4.7.1)

4.1.1.

(1) N 耗尽型. $V_{TN} = -3V$.(2) P 耗尽型. $V_{TP} = 2V$.(3) P 增强型. $V_{TP} = -4V$.

4.2.1.

(1).

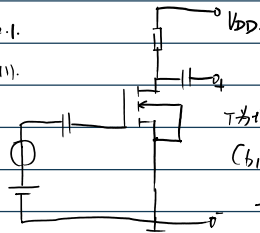


T 为耗尽型 NMOS.

(C1 使得 V_{GS} 无交流栅极.

无交流放大.


(2).

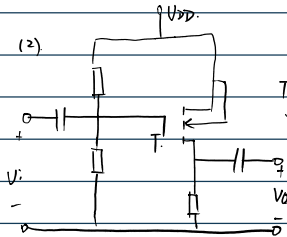

T 为增强型 PMOS.


源极电位有交流放大作用.

(3).

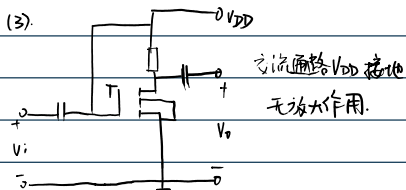交流通路 V_{DD} 接地

无放大作用.

(4).

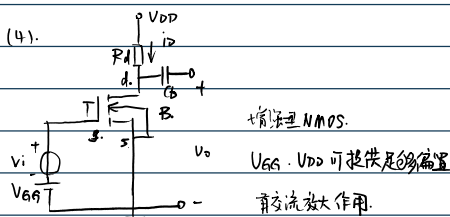


增强型 NMOS.

 V_{GS} 、 V_{DD} 可提供足够偏置

有交流放大作用.

(5).

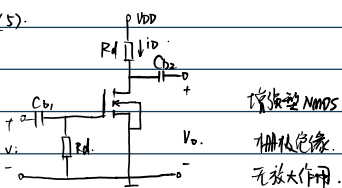


增强型 NMOS


栅极绝缘.

无放大作用.

4.4.3.

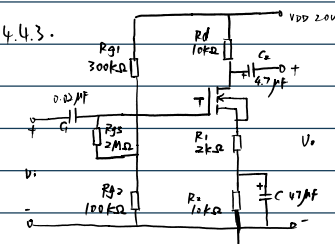


(1). 信号通路: C 短路.

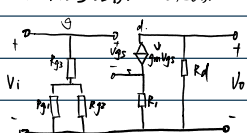(2). $V_o = -g_m V_{GS} R_d$. $V_i = V_{GS} + g_m V_{GS} R_s$.

$$\therefore A_v = \frac{V_o}{V_i} = \frac{-g_m V_{GS} R_d}{V_{GS} + g_m V_{GS} R_s} = \frac{-g_m R_d}{1 + g_m R_s} = \frac{-10}{1 + 1} = -5$$

4.5.2.

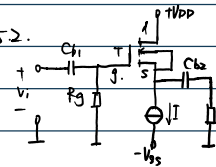 $k_n = 1 \text{ mA/V}^2$ $R_g = 5 \times 10^5 \Omega$ $V_{TN} = 1.2 \text{ V}$ $R_L = 4 \times 10^3 \Omega$ $\lambda = 0$ $I = 1 \times 10^{-3} \text{ A}$ $V_{DD} = V_{SS} = 5 \text{ V}$

$$I = I_{DQ} = k_n (V_{GSQ} - V_{TN})^2 = (V_{GSQ} - 1.2)^2 \times 10^{-3}$$

$$(V_{GSQ} - 1.2)^2 = 1$$

$$V_{GSQ} - 1.2 = \pm 1$$

$$V_{GSQ} = 2.2 \text{ V}$$

$$V_{DSQ} = V_D - V_S = 7.2 \text{ V}$$


$$V_{DSQ} > V_{GSQ} - V_{TN} > 0 \therefore \text{恒流区}$$

$$g_m = 2 \sqrt{k_n I_{DQ}} = 2 \times 10^{-3} \text{ S}$$

$$A = \frac{V_o}{V_i} = \frac{g_m V_{GS} R_L}{g_m V_{GS} R_L + V_{GS}} = \frac{g_m R_L}{g_m R_L + 1} = \frac{8}{9} \approx 0.89$$

$$R_o = \frac{1}{g_m} = 0.5 \text{ k}\Omega$$

4.5.5.

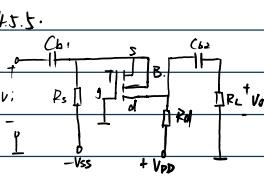 $V_{DD} = V_{SS} = 5 \text{ V}$ $V_{TN} = 1 \text{ V}$ $R_s = 10^4 \Omega$ $\lambda = 0$ $R_d = 5 \times 10^3 \Omega$ $R_L = 5 \times 10^3 \Omega$ $k_n = 3 \times 10^{-3} \text{ A/V}^2$

$$(1) \begin{cases} I_{DQ} = k_n (V_{GSQ} - V_{TN})^2 & \text{--- ①} \\ -V_{SS} + I_{DQ} R_s + V_{GSQ} = 0 & \text{--- ②} \end{cases}$$

$$\text{由 ②: } V_{GSQ} = 5 - I_{DQ} R_s$$

$$\therefore I_{DQ} = 3 \times (5 - 10^4 I_{DQ} - 1)^2$$

$$3 \times (16 + 100 I_{DQ}^2 - 80 I_{DQ})$$

$$300 I_{DQ}^2 - 240 I_{DQ} + 48 = 0$$

$$I_{DQ} = \frac{241 \pm \sqrt{481}}{600} \approx \frac{241 \pm 21.93}{600}$$

$$I_{DQ1} \approx 0.438 \quad I_{DQ2} \approx 0.367$$

$$\therefore V_{GSQ} = 5 - 10 I_{DQ} \approx 1.33 \text{ V}$$

$$\therefore V_S = 0 - V_{GSQ} = -1.33 \text{ V}$$

$$\therefore V_{DSQ} = V_D - V_S = V_{DD} - I_{DQ} R_d - V_S$$


$$\approx 4.495 \text{ V}$$

$$V_{DSQ} > V_{GSQ} - V_{TN} > 0$$

$$(2) g_m = 2 k_n (V_{GSQ} - V_{TN}) \approx 1.98 \times 10^{-3} \text{ S}$$

$$(3) A_v = \frac{V_o}{V_i} = g_m \cdot \frac{R_d R_L}{R_d + R_L} = 1.98 \times 10^{-3} \times 2.5 \times 10^3 = 4.95$$

4.7.1

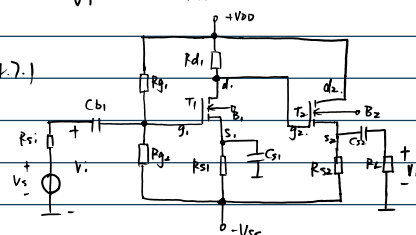 $R_L = 5 \text{ k}\Omega$ $k_{n1} = k_{n2} = 1 \text{ mA/V}^2$ $R_{d1} = 3 \text{ k}\Omega$ $V_{TN1} = V_{TN2} = 1.5 \text{ V}$ $R_{s1} = 20 \text{ k}\Omega$ $\lambda_1 = \lambda_2 = 0$ $R_{s2} = 5 \text{ k}\Omega$ $R_{g1} = 300 \text{ k}\Omega$ $R_{g2} = 300 \text{ k}\Omega$ $V_{GS10} = V_{GS20} = 3 \text{ V}$

$$V_i = V_{gs} + g_m V_{gs} R_i$$



$$\therefore A_i = \frac{V_o}{V_i} = \frac{-g_m V_{gs} R_d}{V_{gs} + g_m V_{gs} R_i} = \frac{-g_m R_d}{1 + g_m R_i} = \frac{-10}{1+2} = -3.3$$

$$(3) \quad R_i = R_{g1} + \frac{R_{g1} R_{g2}}{R_{g1} + R_{g2}} = 10^6 + \frac{3 \times 10^3 \times 10^3}{4 \times 10^3} = 207.5 \text{ k}\Omega$$



(4) ?

4.4.4


(1)

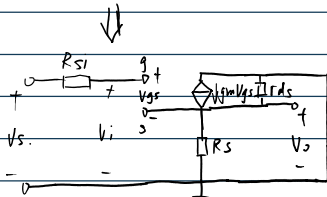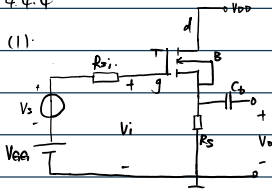



(2)

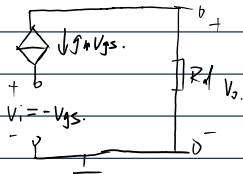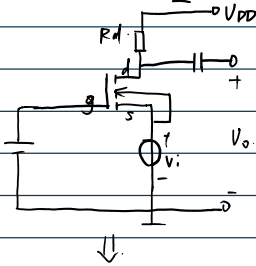

(3)

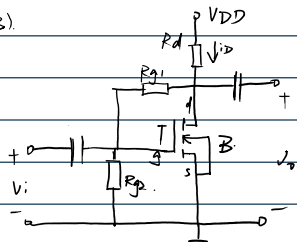

↓

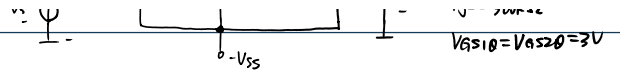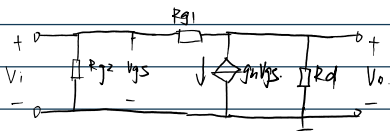

(1)

$$g_{m1} = g_{m2} = 2k_n (V_{GS10} - V_{TN1}) = 3 \times 10^{-3} \text{ S}$$

$$R_i = \frac{5 \times 3 \times 10^3}{5 + 3} = 187.5 \times 10^3 \Omega$$

$$R_o = R_{s2} \parallel \frac{1}{g_m} \parallel R_{s2} = R_{s2} \parallel \frac{1}{g_m}$$

$$= \frac{1}{\frac{1}{5 \times 10^3} + 3 \times 10^{-3}} = 312.5 \Omega$$

$$(2) \quad A_v = \frac{V_o}{V_i} = - \frac{g_{m1} g_{m2} R_{s2}}{1 + g_{m2} \frac{R_{s2} R_L}{R_{s2} + R_L}} \approx -8.735$$

$$\therefore A_{us} = A_v \cdot \frac{R_i}{R_i + R_{s1}} = -8.735 \times 0.9056 \approx -7.893$$

模电作业.5

2025年10月29日 23:47

5.1.1 5.2.1 5.2.9 5.2.12 5.4.4

5.1.1


已知 C 为基极;

$$V_C - V_B = -0.2 < 0.$$


∴ B 为发射极

∴ A 为集电极; PNP

5.2.12.

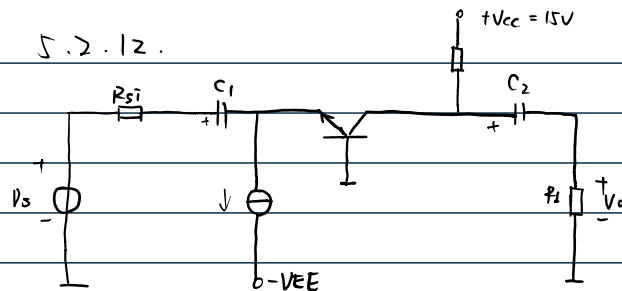


5.2.1

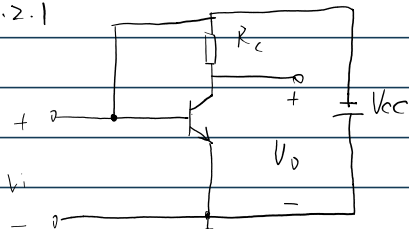


交流时 Vi 补径路

∴ 无交流放大

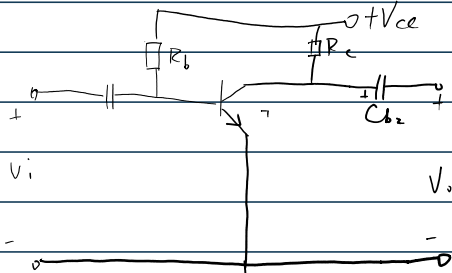


有交流放大

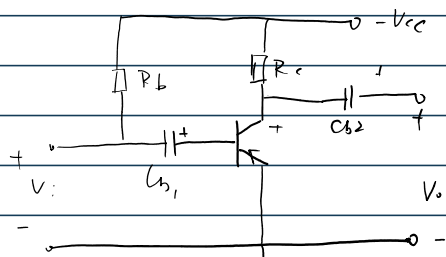

Cb1 阻断直流通路


∴ 交流无放大作用

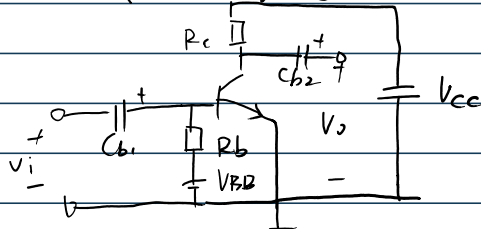

∴ Cb1 阻断基极

∴ 无放大

5.4.4

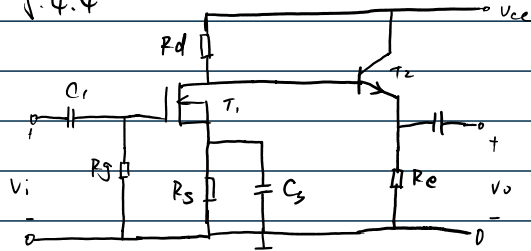



$$A_{v1} = -g_{m1} \cdot R_{L1} \quad A_{v2} = \frac{(1+\beta) R_e}{(1+\beta) R_e + r_{be}}$$

$$A_v = A_{v1} A_{v2} = -\frac{g_{m1} (1+\beta) R_e R_d}{r_{be} + R_d + (1+\beta) R_e}$$

$$P_i = R_g \quad P_o = \frac{(R_d + r_{be}) R_e}{R_e (1+\beta) + R_d + r_{be}}$$

5.2.7)

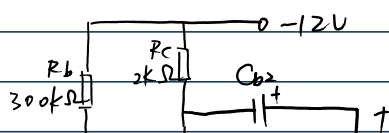

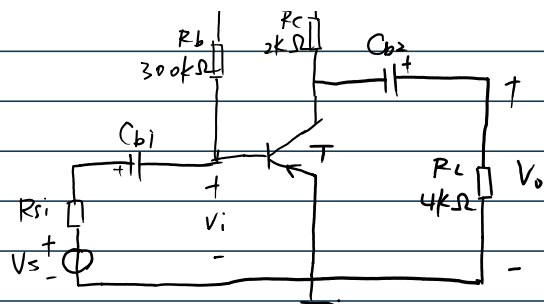


$$(1) \quad I_{BQ} = \frac{-V_{BEQ} + V_{CC}}{R_b} \approx 40 \mu A.$$

$$I_{CQ} = \beta I_{BQ} \approx 4 mA$$

$$V_{CEQ} \approx -12 + R_c \cdot I_{CQ} \approx -4 V.$$

(2).

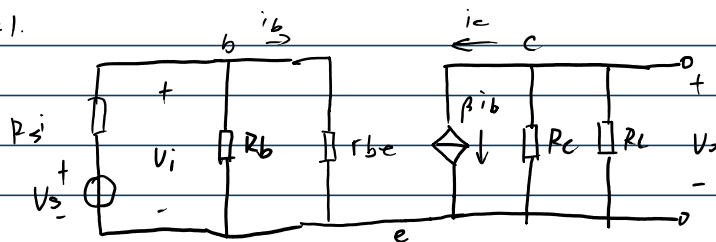



$$(3). \quad r_{be} = 200 + (\beta + 1) \frac{V_T}{I_{CQ}} \approx 857 \Omega.$$

$$A_v = \frac{V_o}{V_i} \approx -155.7$$

$$R_i = \frac{\beta r_{be}}{R_b + r_{be}} \approx 855 \Omega.$$

$$R_o \approx R_c = 2 k\Omega.$$

(4) ~~截止失真~~ ~~交流 \$R_L\$~~

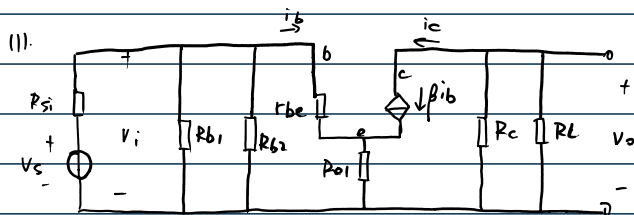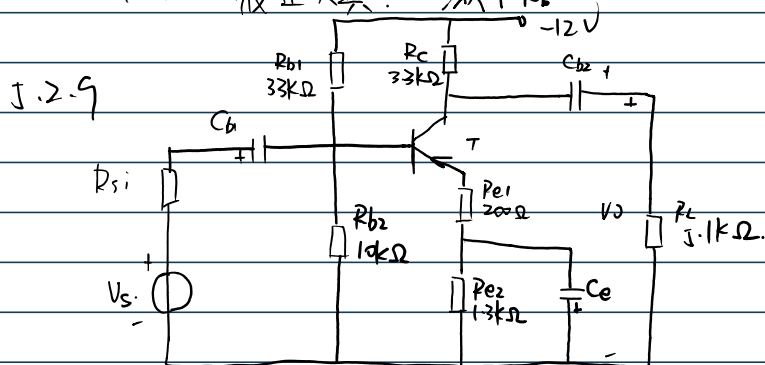

$$(2). \quad V_{BQ} = \frac{R_{b2}}{R_{b1} + R_{b2}} \cdot (-12) \approx -2.8 V.$$

$$I_{EQ} = \frac{-V_{EQ}}{R_{e1} + R_{e2}} = 1.4 \times 10^{-3} A.$$

$$\therefore r_{be} = 1147 \Omega$$

$$R_i = 4.6 k\Omega \quad R_o \approx R_c = 3.3 k\Omega$$

$$(3) \quad A_{vs} = \frac{V_o}{V_s} \approx -7.8$$

$$V_o = A_{vs} \cdot V_s \approx -117 \text{ mV} \times 10^{-3} \text{ V}$$


(4).

2025年11月8日

20:03

6.1.3. 6.3.1. 6.3.2.

6.1.3.

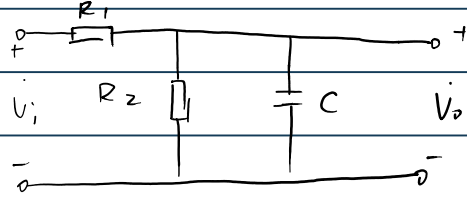

(1). 分压通路

$$(2). A_v = \frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + j\omega C \frac{R_1 R_2}{R_1 + R_2}} = \frac{R_2}{R_1 + R_2} \cdot \frac{1}{1 + j\frac{\omega}{f_H}}$$

当 $f=0$ 取得最大值 $\frac{10}{11}$

$$(3). f_H = \frac{1}{2\pi C \frac{R_1 R_2}{R_1 + R_2}} = 58.4 \text{ MHz.}$$


6.3.1

$$(1). C = C_{gs} + C_{gd} (1 + g_m R_L) = 3.1 \times 10^{-11} \text{ F.}$$

$$(2). f_H = \frac{1}{2\pi C R_{Si}} = \frac{1}{2\pi \times 3.1 \times 10^{-11} \times R_{Si}} > 10^7 \text{ Hz}$$

$$\therefore R_{Si} < 5.1 \text{ k}\Omega.$$

6.3.2.

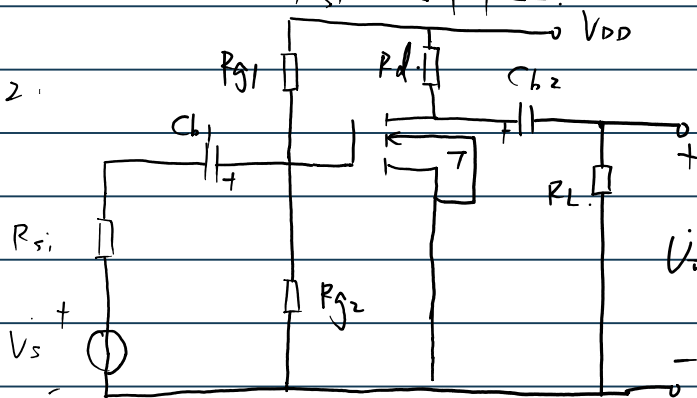

$$V_{GSQ} = \frac{R_{G2}}{R_{G1} + R_{G2}} \cdot V_{DD} \approx 1.7 \text{ V.}$$

 $\therefore V_{DSQ} \approx 3 \text{ V. } I_{DQ} \approx 0.19 \text{ mA}$ 在恒流区.

$$g_m = 2K_n (V_{GSQ} - V_{TN}).$$

$$= 1.12 \text{ mS.}$$

$$R_L' = 7.54 \text{ k}\Omega.$$

$$\therefore A_{vsm} = -g_{m1}' \cdot \frac{R_{g1} // R_{g2}}{R_{s1} + R_{g1} // R_{g2}} \approx -2.65.$$


$$\therefore C = C_{gs} + C_{gd} (1 + g_m R_L') \approx 7.54 \times 10^{-9} \text{ F}.$$

$$R_{s1}' \approx 1.86 \text{ k}\Omega.$$

$$f_H = \frac{1}{2\pi C R_{s1}'} = 33.7 \text{ MHz}$$

2025年11月13日 15:09

7.1.4 7.2.1 7.5.1 7.5.3 7.5.4 7.5.6

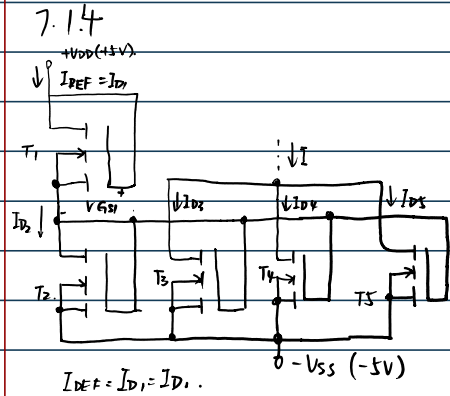

$$\therefore \begin{cases} K_{n1}(V_{GS1} - V_{TN})^2 = K_{n2}(V_{GS2} - V_{TN})^2 \\ V_{DD} + V_{SS} = V_{GS1} + V_{GS2} \end{cases}$$

$$\therefore \begin{cases} 10 = V_{GS1} + V_{GS2} \\ 0.1(V_{GS1} - 2)^2 = 0.25(V_{GS2} - 2)^2 \end{cases}$$

$$\therefore 0.15V_{GS2}^2 + 0.6V_{GS2} - 5.4 = 0$$


$$V_{GS2} = \frac{-0.6 \pm \sqrt{0.36 + 0.6 \times 5.4}}{0.3}$$

$$\therefore V_{GS2} \approx 4.3V$$

$$\therefore V_{GS1} \approx 5.7V$$

$$\therefore I_{REF} = 0.1(V_{GS1} - V_{TN})^2 \approx 1.37mA$$

$$I = 3I_{REF} \approx 4.11mA$$

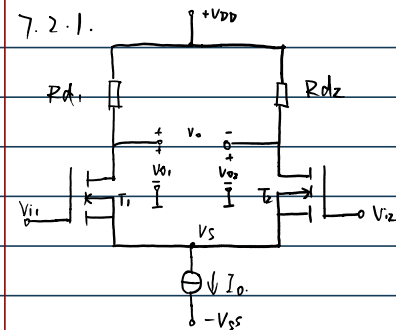

$$V_{GS1} - V_{TN} = \sqrt{\frac{I_{D1}}{K_n}} \approx 0.26V$$

$$V_{D1} = V_{DD} - I_{D1}R_{D1} = 4V$$

$$V_{S1} = -V_{GS1}$$

$$\therefore V_{D1} - V_{S1} = 4 + V_{GS1} = 4 + 0.26 + V_{TN} > 0$$
 恒成立

$\therefore$ 位于恒流区

$$\therefore g_m = \sqrt{2K_n I_{D1}} = 0.77mS$$

$$\therefore A_{vd2} = \frac{V_{o2}}{V_{id}} = \frac{1}{2}g_m R_{D1} \approx 3.9$$

$$A_{vcs} = \frac{V_{o2}}{V_{ic}} \approx -\frac{R_{D1}}{2r_o} = -0.05$$

$$|K_{CMR}| = \left| \frac{A_{vd2}}{A_{vcs}} \right| \approx 78$$

7.5.3.


$$(1) BW = \frac{f_T}{A_v} = \frac{5MHz}{10} = 500kHz$$

$$BW_P = \frac{S_P}{2\pi V_{om}} \approx 1.91 \times 10^5 Hz$$

$$(2) V_{om} = \frac{S_P}{5 \times 2\pi BW_P} \approx 2V$$

$$A_v = \frac{f_T}{1 \times BW_P} \approx 5.24$$

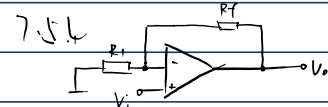
$$\therefore V_{im} = \frac{V_{om}}{A_v} \approx 0.38V$$



$$(1) BW = \frac{f_T}{A_v} = 400MHz$$

$$V_{om} = \frac{S_P}{2\pi BW} = 0.4V$$
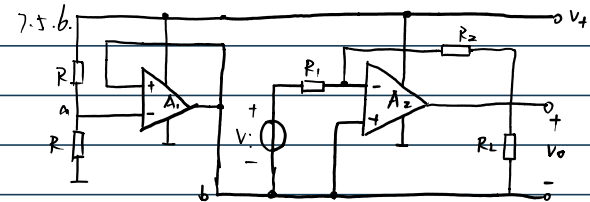
$$(2) BW_P = \frac{S_P}{2\pi V_{om}} \approx 159MHz$$



$$(1) \text{对 } A_2: \frac{V_i}{R_1} = \frac{-V_o}{R_2}$$

$$A_v = -\frac{R_2}{R_1}$$

$$(2) f_T \geq BW|A_v| = 2MHz$$

$$\therefore S_P \geq 2\pi V_{om} \cdot f_{max} = 1.256 V \cdot \mu s^{-1}$$

$$(3) i_{RF} = \frac{V_{om}}{R_2} = 0.1mA$$


$$\therefore I_{Lmax} \leq 10mA$$

$$\therefore i_{omax} = I_{Lmax} + i_{RF} = 10.1mA$$

(4) 不可

连接后可使得 A 的输出电阻逼近 0 接近理想电压源。



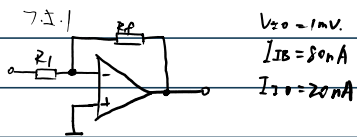

$$(1). V = \left(\frac{R_f}{R_i} + 1 \right) \left[V_{I0} + I_{IB} \cdot \frac{R_i R_f}{R_i + R_f} + \frac{1}{2} I_{I0} \frac{R_i R_f}{R_i + R_f} \right] \approx 11.9\text{mV}$$

$$(2). V = \left(\frac{R_f}{R_i} + 1 \right) \left[V_{I0} + I_{IB} \cdot \frac{R_i R_f}{R_i + R_f} + \frac{1}{2} I_{I0} \frac{R_i R_f}{R_i + R_f} \right] \approx 100.98\text{mV}$$

$$(3). V_f = \left(\frac{R_f}{R_i} + 1 \right) V_{I0} + I_{I0} R_f = 11.2\text{mV}$$

$$V_2 = \left(\frac{R_f}{R_i} + 1 \right) V_{I0} + I_{I0} R_f = 31\text{mV}$$

∴ 小电阻时, 平衡电阻对于减小误差作用更不明显.

2025年11月22日 18:59

8.1.1. 8.1.2. 8.3.5 8.4.1 8.4.5 8.5.2.

8.1.1.

a. R_1, R_2 组成反馈网络, V_o 在 R_1 压降为反馈电压.

负反馈, 直流反馈和交流反馈.

b. A_2, R_3 组成反馈通路. A_2 电压跟随器.

负反馈, 直流反馈和交流反馈.

c. R_1 组成反馈网络, i_o 在 R_1 压降为反馈电压.

负反馈, 直流反馈和交流反馈.

d. R_1, R_2 组成反馈网络.







负反馈, 直流反馈和交流反馈.

e. R_f 组成反馈网络.

负反馈, 直流反馈和交流反馈.


f. R_{o1} 组成反馈网络.

负反馈, 直流反馈和交流反馈.

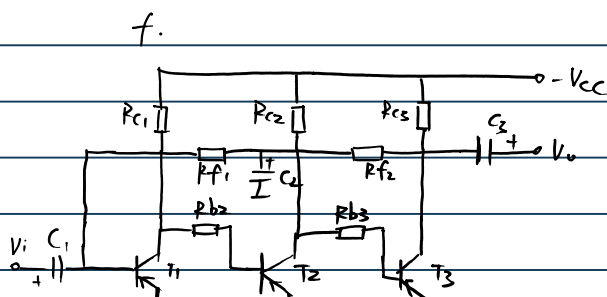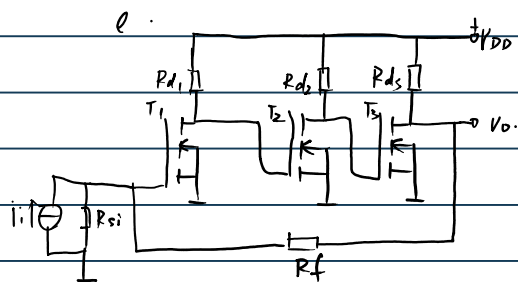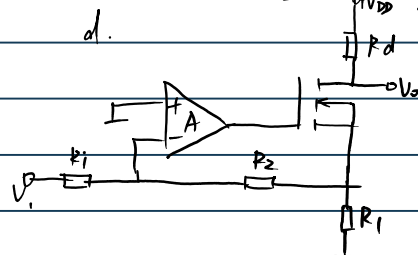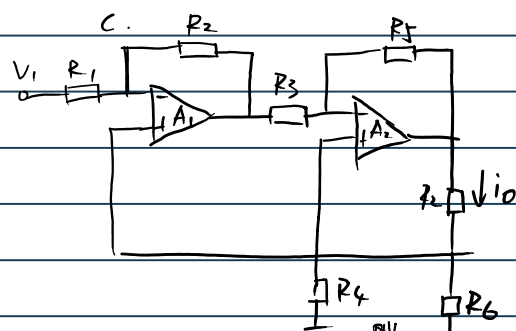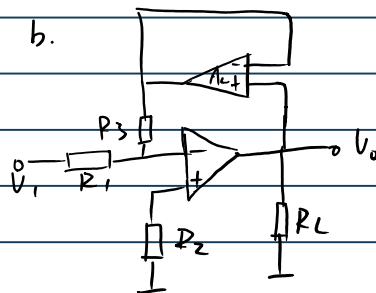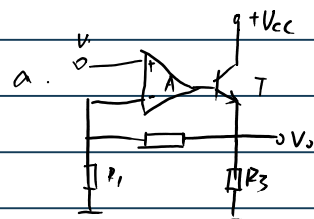


8.1.2.

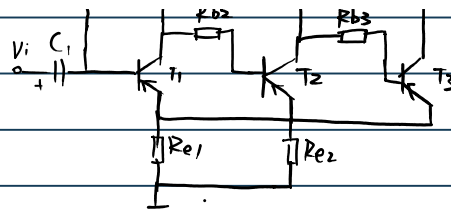a. R_1, R_2 串联负反馈.b. A_2, R_3 并联负反馈.c. R_6 串联负反馈.d. R_1, R_2 并联负反馈.e. R_f 并联负反馈.f. R_{e1} 串联负反馈.




8.3.5.

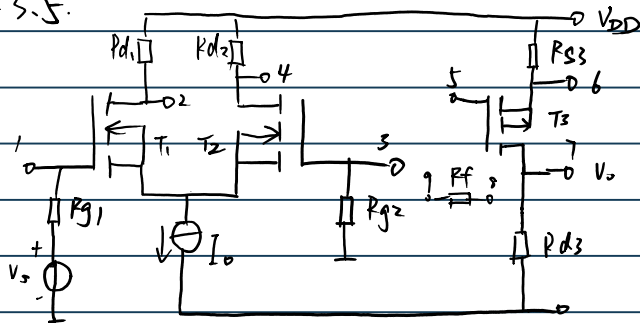


- (1). 6-8 9-1 5-2.
- (2). 7-8 3-9. 2-5.
- (3). 7-8. 1-9. 4-5
- (4). 6-8 3-9. 4-5

8.4.1

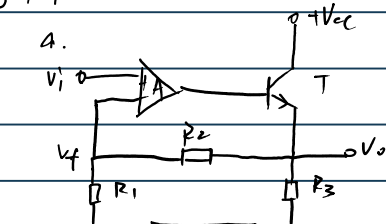

$$a. V_i \approx V_f = \frac{R_1}{R_1 + R_2} V_o$$

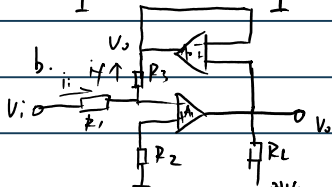
$$\therefore A_{vf} = \frac{V_o}{V_i} \approx 1 + \frac{R_2}{R_1}$$



$$b. i_i = i_f = -\frac{V_o}{R_3}$$

$$A_{vf} = \frac{V_o}{i_i} \approx -R_3$$
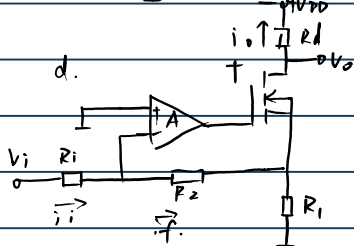
$$A_{vf} = \frac{V_o}{V_i} = \frac{V_o}{i_i R_1} \approx -\frac{R_3}{R_1}$$




$$d. F_i = \frac{i_f}{i_o} \approx \frac{R_1}{R_1 + R_2}$$


$$A_{if} = \frac{i_o}{i_f} \approx 1 + \frac{R_2}{R_1}$$

$$e. A_{rf} = \frac{V_o}{i_i} = -\frac{i_f R_f}{i_i} \approx -R_f$$

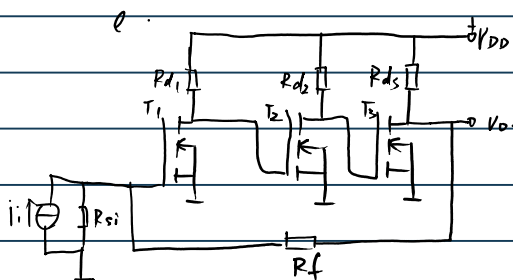
$$A_{vf} = \frac{V_o}{V_i} \approx -\frac{R_f}{R_{s1}}$$


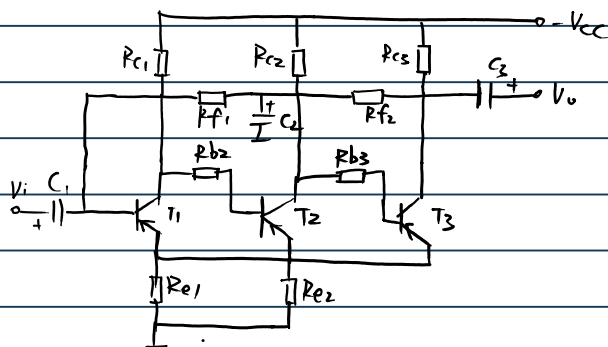
$$f. A_{gf} = \frac{i_o}{V_i} = \frac{1}{R_{e1}}$$


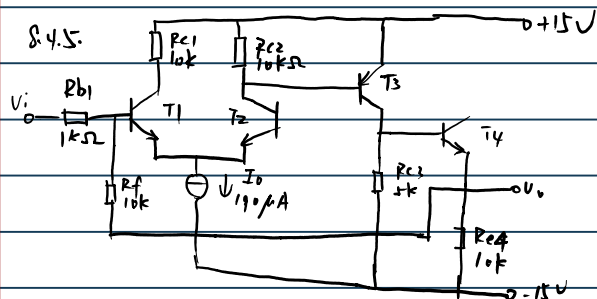
$$A_{vf} = \frac{V_o}{V_i} \approx - \frac{\beta R_{c3} R_{f2}}{R_{e1}(R_{c3} + R_{f2})}$$




(1). $\frac{V_i}{R_{f1}} \approx \frac{-V_o}{R_{f2}}$ $V_{b1} = V_{b2} = 0$
 $i_{b1} = 0$

$\therefore A_{vf} = -10$

(2). T_2 基极用 R_{b2} 接到输入端.
 T_1 基极用 R_{b1} 接地.

(3). $A_{vf} \approx 1 + \frac{R_f}{R_{b1}} \approx 11$

8.5.2.

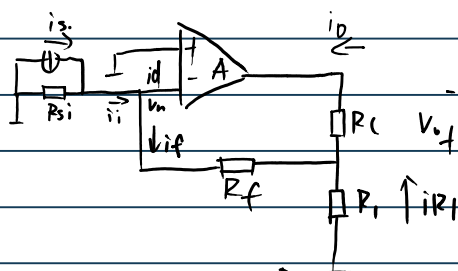


$$i_i \approx i_f \approx \frac{R_1}{R_1 + R_f} i_o$$

$\therefore A_{if} = 10$

$\therefore R_f = 9R_1$

2025年12月4日 19:29

10.8.1 10.8.6 10.8.8

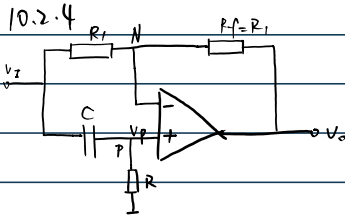

$$(1) \frac{V_i(j\omega) - V_n(j\omega)}{R_1} = \frac{V_n(j\omega) - V_o(j\omega)}{R_1}$$

$$V_n(j\omega) = V_p(j\omega)$$


$$\frac{V_i(j\omega) - V_p(j\omega)}{\frac{1}{j\omega C}} = \frac{V_p(j\omega)}{R}$$

$$\therefore \frac{V_i(j\omega)}{1+j\omega RC} = \frac{V_i(j\omega) + V_o(j\omega)}{2+j\omega RC}$$

$$\therefore A_v(j\omega) = -\frac{1-j\omega RC}{1+j\omega RC}$$

$$(2) |A_v(j\omega)| = \sqrt{\frac{1+(\omega RC)^2}{1+(\omega RC)^2}} = 1$$


$$\varphi = -\pi - 2\arctan(\omega RC)$$

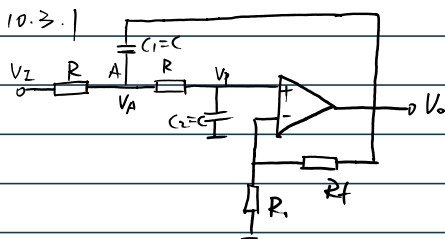

$$A(s) = \frac{V_o(s)}{V_i(s)} = \frac{A_{vf}}{1 + (sRC)^2 + (3-A_{vf})sRC} = \frac{A_o}{1 + \left(\frac{s}{\omega_c}\right)^2 + Q\left(\frac{s}{\omega_c}\right)}$$

$$\therefore \omega_c = \frac{1}{RC} = 100 \text{ rad/s} \quad Q = \frac{1}{3-A_{vf}} = 0.707$$

$$20\lg|A_o| = 40 \text{ dB}$$

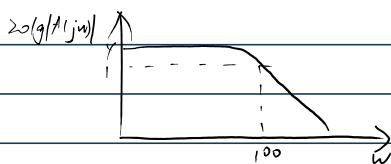

12.6.1


(1). 当 \$T_1\$ 栅极为正, 则 \$T_2\$ 栅极为负 \$\varphi_a = 180^\circ\$, 反馈到 \$T_1\$ 栅极为负

\$\therefore \varphi_a + \varphi_f \neq 0\$ 且 \$\neq 360^\circ\$, 故不能振荡

(2) \$P\$ 为正, \$V_o\$ 为正, \$\varphi_a = 0\$ 或 \$360^\circ\$. 在 \$\omega = \omega_0 = \frac{1}{RC}\$ 时 \$\varphi_f = 0^\circ\$.

\$\therefore\$ 经 \$RC\$ 网络取反网络到同相端信号也为正. \$\varphi_a + \varphi_f = 0\$ 或 \$360^\circ\$. 可振荡

10.8.1

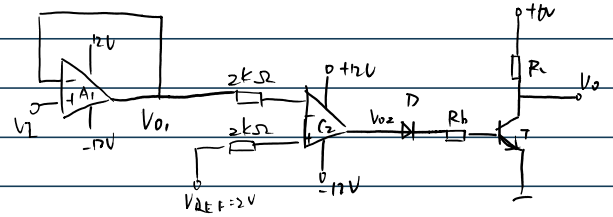

$$(1) I_B = \frac{V_{o2} - V_{BE}}{R_b} \approx 222 \mu A$$





$$I_{BS} = \frac{I_{CS}}{\beta} = \frac{V_{CC} - V_{CES}}{\beta \cdot R_c} \approx 23.5 \mu A$$

$$\therefore I_B \gg I_{BS} \quad \therefore V_{CES} = 0 \quad V_o = 0$$

$$(2) V_i = 3, V_{o1} = 3$$

$$\therefore V_{o1} > V_{REF}. \quad V_{o2} \approx -12V. \quad V_o = 6V.$$

$$(3) V_i = 5 \sin \omega t$$

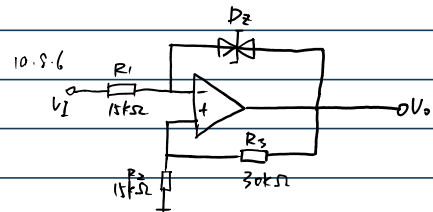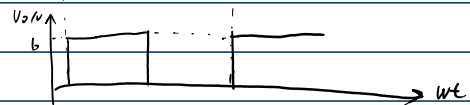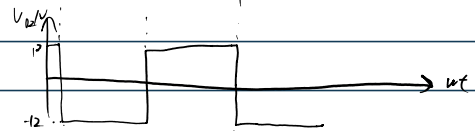
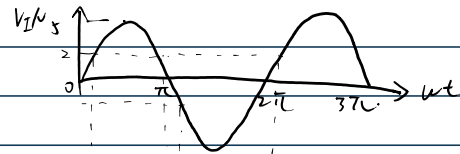


$$(1) F = \frac{V_p}{V_o} = \frac{R_2}{R_2 + R_3} = \frac{1}{3}$$



$$V_N = V_P = \frac{V_o}{3}$$

$$\therefore V_o = \frac{V_o}{3} + V_{Z2} = 9V$$

$$\therefore D_2 \text{ 截止, } V_o = 9V$$

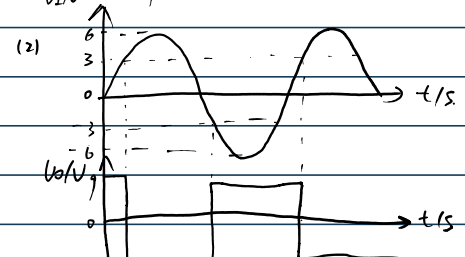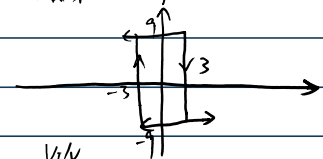

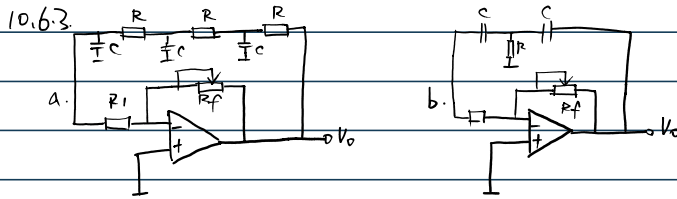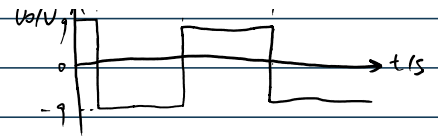$\therefore$ 经RC网络后同相端信号也为正。 $\varphi_a + \varphi_f = 0$ 或 $\pm 360^\circ$ 。可振荡




- a. 运放电路构成反相比例放大; 输入输出 相位差 180° .
 $\Rightarrow$ 三阶RC可 270° . $\therefore$ 存在 f_0 使得 $\varphi_a + \varphi_f = 360^\circ$ 可以振荡.
 b. 二阶RC可 180° , $180^\circ + 180^\circ = 360^\circ$ 因为二阶RC无法达到 180° 所以不振荡

10.8.8


(1) A_1 : RC桥式正弦波振荡电路.

A_2 : 过零比较器.

A_3 : 积分电路.

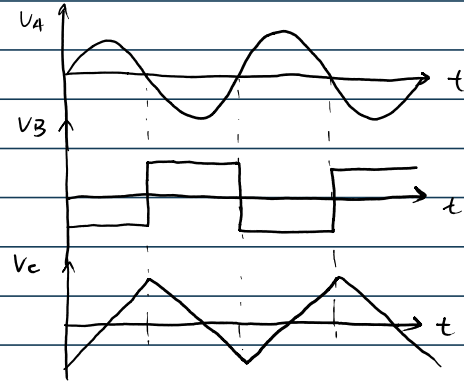

10.6.5

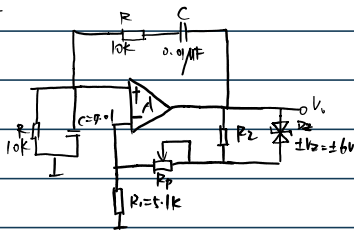

(1) 如图

(2) $|A\dot{F}| > 1$.

$$\omega = \omega_0, |F| = \frac{1}{3}.$$

$$\therefore 1 + \frac{R_2 + R_3}{R_1} > 3.$$

$$\therefore R_2 + R_3 > 10.2 \text{ k}\Omega.$$

$$(3) f = \frac{1}{2\pi RC} = 1592 \text{ Hz}.$$

$$(4) \text{ 稳定时, 有 } A\dot{U} = 3 \quad F\dot{U} = \frac{1}{3}.$$

$$\omega = \omega_0 = \frac{1}{RC}$$

$$U_N = U_P = \frac{1}{3} U_{om}.$$

$$\therefore U_{RP} + U_Z = \frac{2}{3} U_{om}.$$

$$\therefore U_{RP} + U_Z = \frac{2}{3} U_{om}$$

$$\therefore U_{RP} = \frac{U_{om} R_2}{R_1 + R_2}.$$

$$\therefore U_{RP} = \frac{U_{om} R_2}{3 R_1}.$$

$$\frac{U_{om} R_2}{3 R_1} + U_Z = \frac{2}{3} U_{om}.$$

$$U_{om} = \frac{3 R_1}{2 R_1 + R_2} \cdot \frac{1}{2}.$$