

附录 1: 参考公式

$$i_D = I_S (e^{\frac{v_D}{V_T}} - 1) \quad r_D = \frac{V_T}{I_D} \quad i_D = K_n (v_{GS} - V_{TN})^2$$

$$i_D \approx 2K_n (v_{GS} - V_{TN}) v_{DS} \quad K_n = \frac{K'_n}{2} \cdot \frac{W}{L} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)$$

$$i_D = K_n (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS}) \quad r_{ds} = [\lambda K_n (v_{GS} - V_{TN})^2]^{-1} = \frac{1}{\lambda I_D}$$

$$g_m = 2K_n (V_{GSQ} - V_{TN}) = 2\sqrt{K_n I_{DQ}} = \frac{2}{V_{TN}} \sqrt{I_{DQ} I_D} \quad R_o = R // r_{ds} // \frac{1}{g_m} \quad \left(\begin{array}{l} \text{mos} \\ \text{共源放大} \end{array} \right)$$

(低频响应) $r_{be} = 200 + (1 + \beta) \frac{26(\text{mV})}{I_{EQ}(\text{mA})}$ (BJT)

高通旁路

电容对应
下限频率

$$f_{L2} = \frac{g_m}{2\pi C_s}$$

$$f_H = \frac{1}{2\pi R'_s C}, \quad C = C_{gs} + (1 + g_m R'_L) C_{gd}, \quad R'_s = R_s // R_g$$

高频响应 (MOS管)

差模电压增益 (双端输入单端输出)

① 输出是 V_{o1} (空的那一边)
如是一边的则打“-”

② 输出有负载, 再并上 R_L
③ 双端输出增益 $\times 2$, 有负载并上

$$A_{vd1} = -\frac{g_m (r_{ds} // R_d)}{2}$$

$$A_{vc1} = -\frac{g_m (r_{ds} // R_d)}{1 + g_m (2r_o)}$$

$$K_{CMR1} \approx \frac{g_m r_o}{A_{vc1}} \rightarrow \text{单端输出的共模抑制比}$$

$$A_{vd1} = -\frac{\beta R_c}{2r_{be}}$$

$$A_{vc1} = \frac{-\beta R_c}{r_{be} + (1 + \beta) 2r_o}$$

$$K_{CMR1} \approx \frac{\beta r_o}{r_{be}}$$

共模输入电阻 (射极耦合差分放大)

$$R_{ic} = \frac{1}{2} [r_{\pi} + (1 + \beta)(2r_o)]$$

r_o 一般是电流源的
动态等效电阻

$$V_O = (1 + R_f / R_1) \left[V_{IO} + I_{IB} (R_1 // R_f - R_2) + \frac{1}{2} I_{IO} (R_1 // R_f + R_2) \right]$$

开环闭环增益 $A_f = \frac{A}{1 + AF}$

$$P_{om} = \frac{1}{2} \cdot \frac{V_{om}^2}{R_L} \approx \frac{1}{2} \cdot \frac{V_{CC}^2}{R_L}$$

$$P_V = \frac{2V_{CC} V_{om}}{\pi R_L} \approx \frac{2}{\pi} \cdot \frac{V_{CC}^2}{R_L}$$

直流电源的供给功率

RC 振荡电路反馈系数

$$\dot{F}_V = \frac{j\omega RC}{(1 - \omega^2 R^2 C^2) + j3\omega RC}$$

$$\dot{F}_V = \frac{1}{3 + j \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)} \quad (\omega_0 = \frac{1}{RC})$$

$$\underline{V_L} = (1.1 \sim 1.2) \underline{V_2} \quad \underline{I_L} = \frac{0.9 V_2}{R_L}$$

平均 D_1, D_2 电流为 $\frac{I_L}{2}$