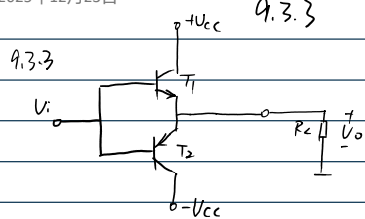


2025年12月23日

21:24

9.3.3

9.4.5



$$(1) P_{om} = \frac{1}{2} \frac{V_{cc}^2}{R_L}$$

$$V_{cc} = 12V$$

$$(2) I_{cm} \geq \frac{V_{cc}}{R_L} = \frac{12}{8} = 1.5A$$

$$|V_{(B*)CEQ}| \geq 2V_{cc} = 24V$$


$$(3) P_V = \frac{2V_{cc}^2}{\pi R_L} = \frac{2 \times 12^2}{8\pi} = \frac{36}{\pi}$$

$$(4) P_{cm}$$

$$P_{cm} \geq 0.2 P_{om} = 1.8W$$

$$(5) V_i \approx V_o \approx \frac{1}{\sqrt{2}} V_{cc} = 6\sqrt{2}V$$

9.4.5

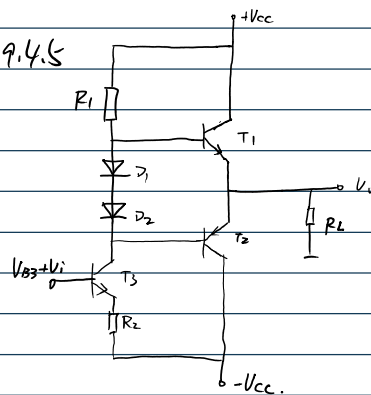

$$P_o, P_V, P_T, \eta$$

$$P_o = \frac{V_o^2}{R_L} = \frac{16^2}{8} = 16W$$

$$P_T = \frac{2}{\pi} \cdot \left(\frac{V_{cc} V_{om}}{\pi} - \frac{V_{om}^2}{4} \right) = 5.6W$$

$$\therefore P_V = P_o + P_T = 21.6W$$

$$\therefore \eta = \frac{P_o}{P_V} = \frac{16}{21.6} \times 100\% = 74.1\%$$